



CS 240 – Computer Architecture

Fall 2024

Lab 4:

RISC-V Decoder

&

Verilog Module Implementation

Concepts

Hardware Description Language

Hardware Description Languages are special languages used to define internal signals and behavior of digital hardware. Some of the very common HDL are Verilog, VHDL and SystemVerilog.


HDLs allow users to easily perform low-level operations over signals like bit manipulations or bit-level arithmetic and logical operations.

Synthesizers

Synthesizers can be considered compilers for HDL. They read HDL code and output a netlist. Netlist is a collection of digital signals, modules, and connections of the related hardware. Like compilers, synthesizers also may warn about possible bugs and unimplementable code. They also perform optimizations over the design.

State machines and Logic Design

 You can imagine digital hardware as a logic cloud that operates on its registers (or memory). Registers hold the current state of your hardware. Depending on the current state and input, your logic will determine the next state.



This type of logic is called a state machine. CPUs work in a similar way. Every cycle they look at their input (instruction) and current state (register file and memory), then determine their next state. Of course, modern CPUs utilize many advanced concepts which makes them more than simple state machines.

Structure of A Verilog File

```
module accumulator(clk, rst, operand, out);  
  input clk, rst;  
  input [31:0] operand;  
  output reg [31:0] out;  
  
  reg [31:0] out_next;  
  
  always @(posedge clk) begin  
    out <= #1 out_next;  
  end  
  
  always @(*) begin  
    out_next = out;  
    if (rst) begin  
      out_next = 0;  
    end else begin  
      out_next = out + operand;  
    end  
  end  
endmodule
```

You can see the structure of a basic accumulator design on the left.

The purple area is where we define the inputs and outputs of the design.

The white area is where we define all internal signals. Both the signals that represent the current state and the next state can be defined here.

The red area is where we represent our register behavior. In most cases, we do not put any extra logic in there. We just represent the transition from the current

state to the next state.

The blue area is where we define all combinational logic. We always modify the signals that represent the next state. Since we only commit our changes at the end of a cycle, any changes to the same signal will override all changes above it. For example, in the above example, if the reset signal is 1, `out_next = 0;` will always override `out_next = out;` logic.

There are two basic variable types in Verilog, `reg` and `wire`. `Reg` does not stand for register. Basically, anything you change inside the `always` blocks should be defined as `reg`. Everything else should be defined as `wire`.

`Always` blocks represent different logic groups inside your hardware. Every `always` block runs in parallel. You cannot modify the same signal from different `always` blocks. This is called a multiple-driver problem. A signal cannot have two values at the same time.

Scope of the Lab

In this assignment, you will implement behavioral logic for two hardware modules in Verilog. For the first task, you will implement a RISC-V Decoder module. The module will only extract related fields and the control signals for each instruction type. The second module will have two different behaviors which will be executed depending on the input signal fetched from the memory. You do not have to worry about memory implementation for this task.

Resources

For this lab, we will use [EDA Playground](#). EDAP is a website that provides both open-source and commercial tools to develop hardware for educational purposes. To access these tools and run your code, you need to register first. To register to EDAP, first, open the home page, then press login. In the login page, you should see an option to register for full access.

Want full access to EDA Playground?

<input type="text"/>
<input type="password"/>
<input type="button" value="Login"/>

[Register for a full account](#) [Forgotten password](#)

To run commercial simulators, you need to register and log in with a username and password for commercial simulators.

If you wish to use EDA Playground as a playground, please log in using your Google account.

On the registration page, enter your information below.

Email (Company or Institution):

To prevent your validation from being disabled, **please supply your company or institution email address. Access will not be granted to freely available email addresses (eg gmail).**

Password:

Company or Institution name:

First name:

Last name:

Job Title:

City:

Country:


To complete your registration, open your email and confirm your email from the registration mail.

You are given the skeleton for each module implementation. You can reach each task from the following links.

Task1: <https://www.edaplayground.com/x/TedX>

Task2: <https://www.edaplayground.com/x/HMgg>

 When you first open these tasks, click the copy button on the top left of the page.



This will create a copy on your account.

Exercise 1

During this lab, you will implement the behavior for RISC_V_Decoder module. This module will take a 32-bit instruction and it will return the related fields for each instruction type.

Instruction types to be decoded:

7 bits	5 bits	5 bits	3 bits	5 bits	7 bits	R-Type I-Type S-Type B-Type J-Type
funct7	rs2	rs1	funct3	rd	op	
imm _{11:0}		rs1	funct3	rd	op	
imm _{11:5}	rs2	rs1	funct3	imm _{4:0}	op	
imm _{12,10:5}	rs2	rs1	funct3	imm _{4:1,11}	op	
imm _{20,10:1,11,19:12}				rd	op	
20 bits				5 bits	7 bits	

You should decode opcode and operand signals for each instruction types (e.g., for I type: opcode, rd, funct3, rs1, imm12).

In addition to opcode and operand signals, you should also decode the main control signals according to the Table 1; and ALU control signals according to Table 2.

Table 1. Main Control Signal Decoder Truth Table

Instruction	Opcode	RegWrite	ImmSrc	ALUSrcA	ALUSrcB	MemWrite	ResultSrc	Branch	ALUOp	Jump
lw (I-type)	0000011	1	00	0	1	0	01	0	00	0
sw (S-type)	0100011	0	01	0	1	1	xx	0	00	0
R-type	0110011	1	xx	0	0	0	00	0	10	0
beq (B-type)	1100011	0	10	0	0	0	xx	1	01	0
I-type ALU	0010011	1	00	0	0	0	00	0	10	0
jal (J-type)	1101111	1	11	x	x	0	10	0	xx	1

Table 2. ALU Control Signal Decoder Truth Table

$ALUOp_{1:0}$	$funct3_{2:0}$	$\{op_5, funct7_5\}$	$ALUControl_{2:0}$	Operation
00	x	x	000	Add
01	x	x	001	Subtract
10	000	00, 01, 10	000	Add
	000	11	001	Subtract
	010	x	101	SLT
	110	x	011	OR
	111	x	010	AND

Below is the test program to test your decoder implementation.

#	RISC-V Assembly	Description	Address	Machine
main:	addi x2, x0, 5	# x2 = 5	0	00500113
	addi x3, x0, 12	# x3 = 12	4	00C00193
	addi x7, x3, -9	# x7 = (12 - 9) = 3	8	FF718393
	or x4, x7, x2	# x4 = (3 OR 5) = 7	C	0023E233
	and x5, x3, x4	# x5 = (12 AND 7) = 4	10	0041F2B3
	add x5, x5, x4	# x5 = (4 + 7) = 11	14	004282B3
	beq x5, x7, end	# shouldn't be taken	18	02728863
	slt x4, x3, x4	# x4 = (12 < 7) = 0	1C	0041A233
	beq x4, x0, around	# should be taken	20	00020463
	addi x5, x0, 0	# shouldn't happen	24	00000293
around:	slt x4, x7, x2	# x4 = (3 < 5) = 1	28	0023A233
	add x7, x4, x5	# x7 = (1 + 11) = 12	2C	005203B3
	sub x7, x7, x2	# x7 = (12 - 5) = 7	30	402383B3
	sw x7, 84(x3)	# [96] = 7	34	0471AA23
	lw x2, 96(x0)	# x2 = [96] = 7	38	06002103
	add x9, x2, x5	# x9 = (7 + 11) = 18	3C	005104B3
	jal x3, end	# jump to end, x3 = 0x44	40	008001EF
	addi x2, x0, 1	# shouldn't happen	44	00100113
end:	add x2, x2, x9	# x2 = (7 + 18) = 25	48	00910133
	sw x2, 0x20(x3)	# mem[100] = 25	4C	0221A023
done:	beq x2, x2, done	# infinite loop	50	00210063

After completing the module, you will first synthesize the module to see if any warnings or errors occur. You can synthesize your module by selecting the Mentor Precision tool from the sidebar, then pressing the Run button.


Tools & Simulators ?

Mentor Precision 2021.1

☐ Show netlist after run

☐ Download files after run

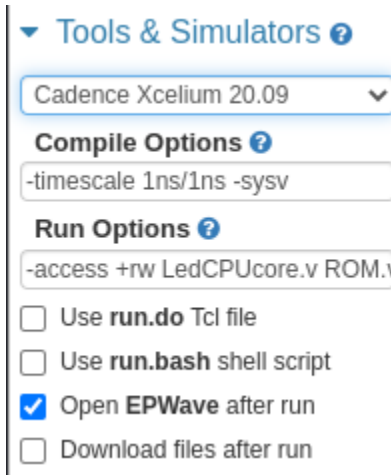After making sure your module synthesizes, you should simulate the module by selecting the Cadence Xcelium tool from the sidebar.



You can also minimize the EPWave window and check if any warnings for wrong values are present in the terminal window. If you have no warnings in the simulation window, it means that you have completed the task.

Exercise 2

You should implement a module that, in every cycle, reads from the memory and changes its behavior depending on the data fetched from the memory. Each data is 16 bits. Your module should read the rightmost 8 bits of the data and change its behavior. If the rightmost 8 bits are not equal to 0, your module should wait up to that many cycles before getting the next line and in the meantime, it should output the leftmost 8 bits. If the rightmost 8 bits are equal to zero, then your module should treat the rightmost 8 bits as an address and change the PC registers value accordingly.

BIT #	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Output	OUTPUT PATTERN								DELAY \neq 0							
Jump	JUMP ADDRESS								DELAY = 0							

So, we have the following logic:

1) DELAY = 0 => Do Jump operation

BIT[15:8] is the address we jump to.

2) DELAY \neq 0 => Do Output operation

BIT[15:8] is the pattern shown in the LEDs.

BIT[7:0] is the amount of time this particular pattern should be shown in the LEDs.

Then it moves to the next address.

The CPU simply starts from address 0 and executes the following instructions.

After completing the module, you should synthesize your code as mentioned above. If you get no warnings, then you should simulate your code. This time, change your simulation options as shown in the following image.

- ☐ Use **run.do** Tcl file
- ☐ Use **run.bash** shell script
- ☐ Open **EPWave** after run
- ☒ Download files after run

This will download a zip file containing project files. Find “dump.vcd” file inside this zip file and open it using GTKWave. Observe the wave form.